


CMOS INVERTER USING CADENCE

Adithyan Anilkumar


2025BEC0014

Git-Hub:- https://github.com/Adithyan-its10/AnalogElectronicsLab_2025BEC0014.git

1. Schematic Design

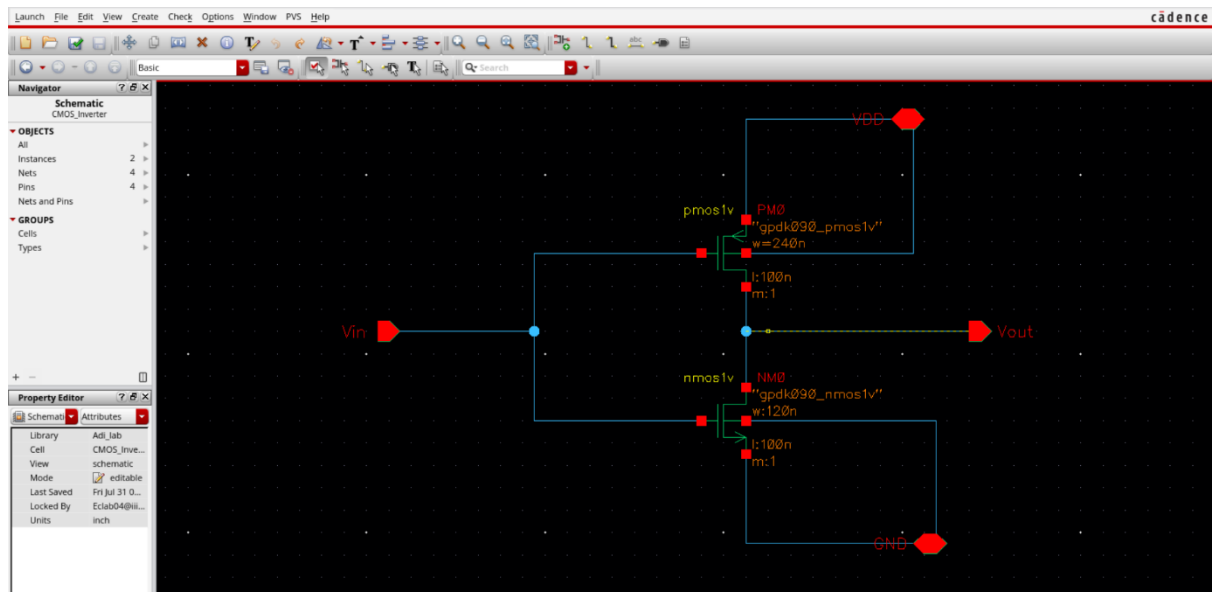

2. Symbol

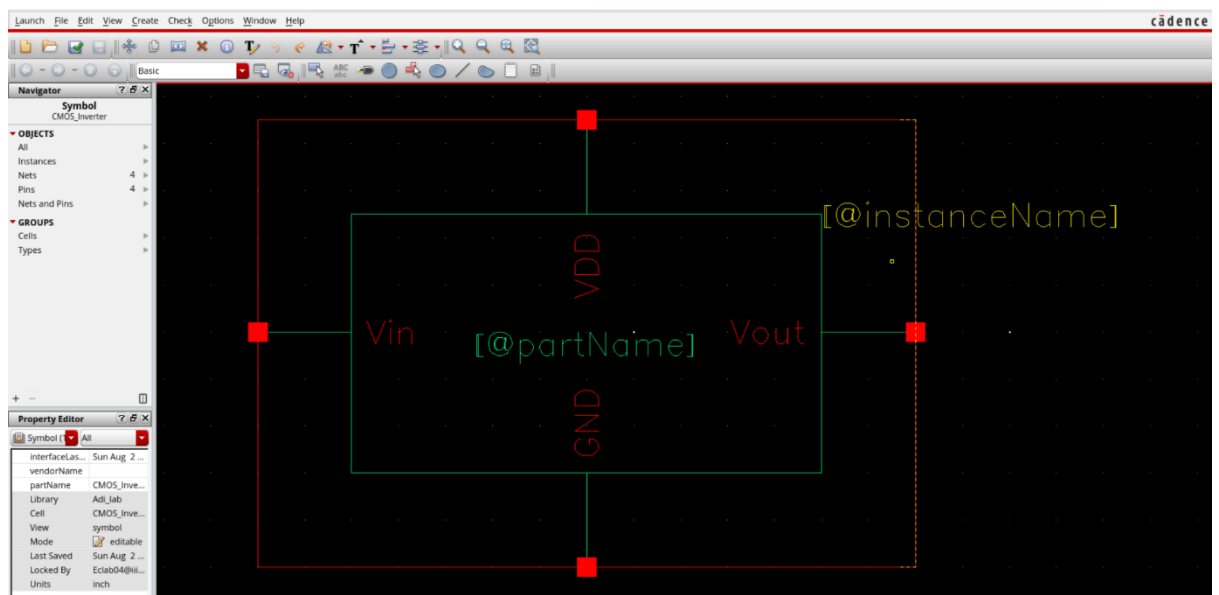

5. Input v/s Output Waveform

