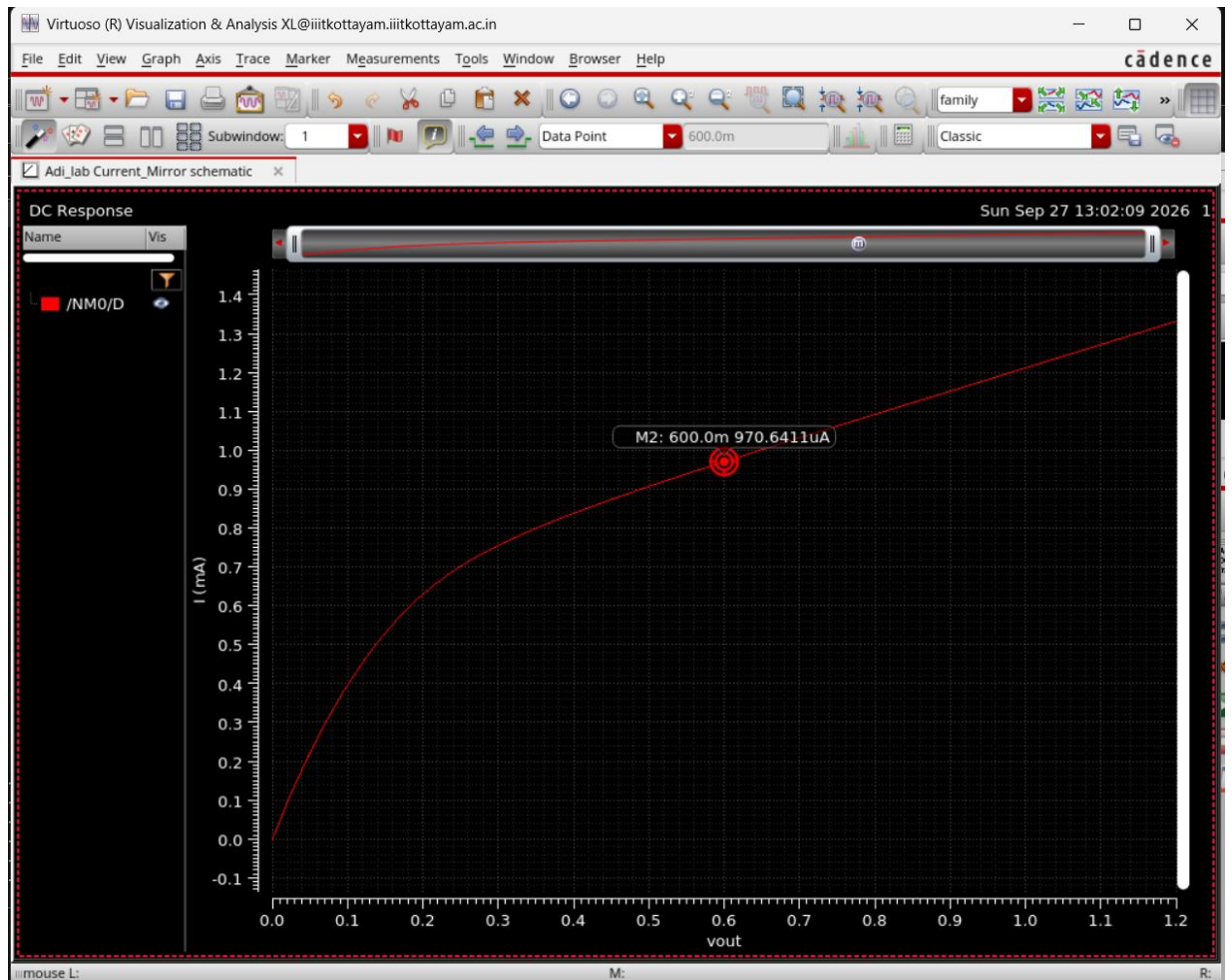



Current Mirror

Adithyan Anilkumar


2025BEC0014


1. Simple Current Mirror



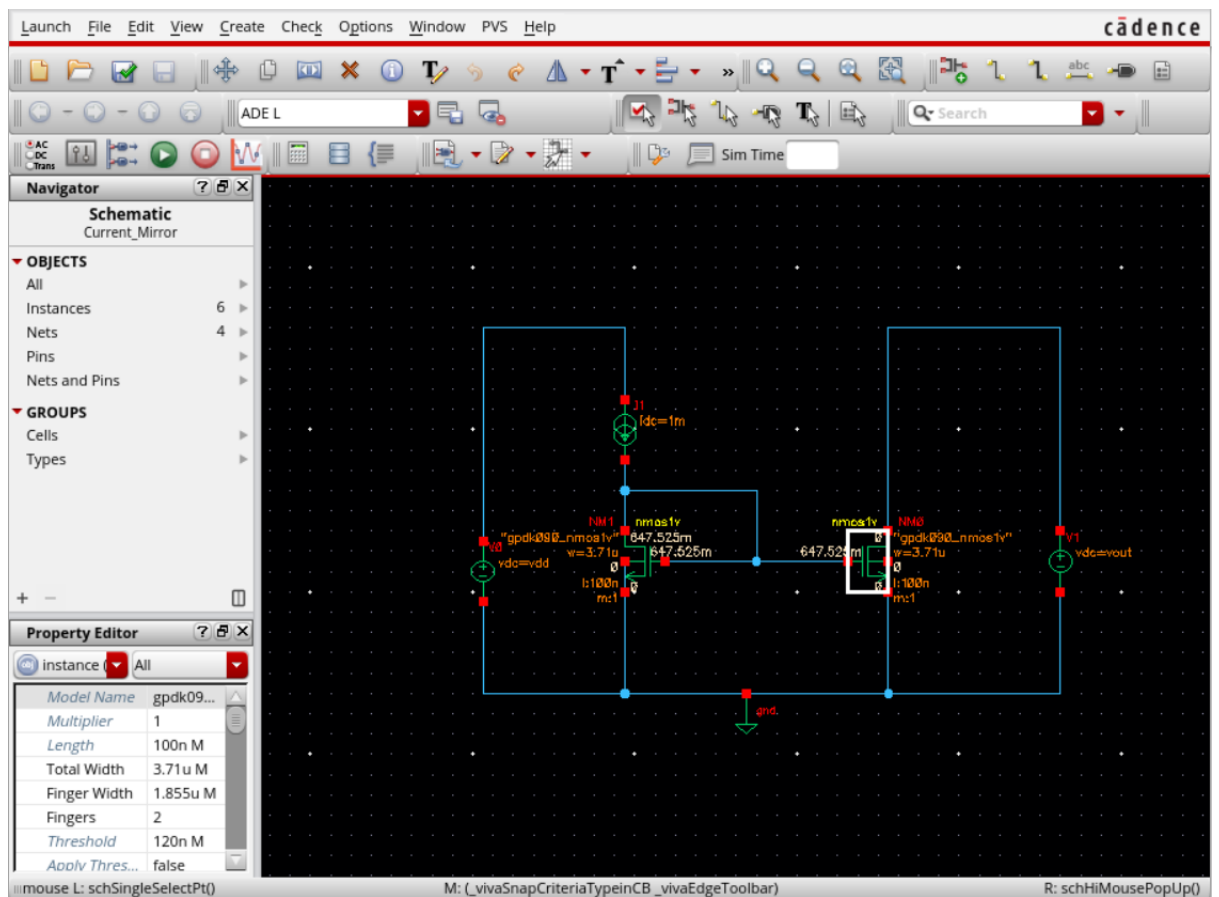



2. Cascode Current Mirror

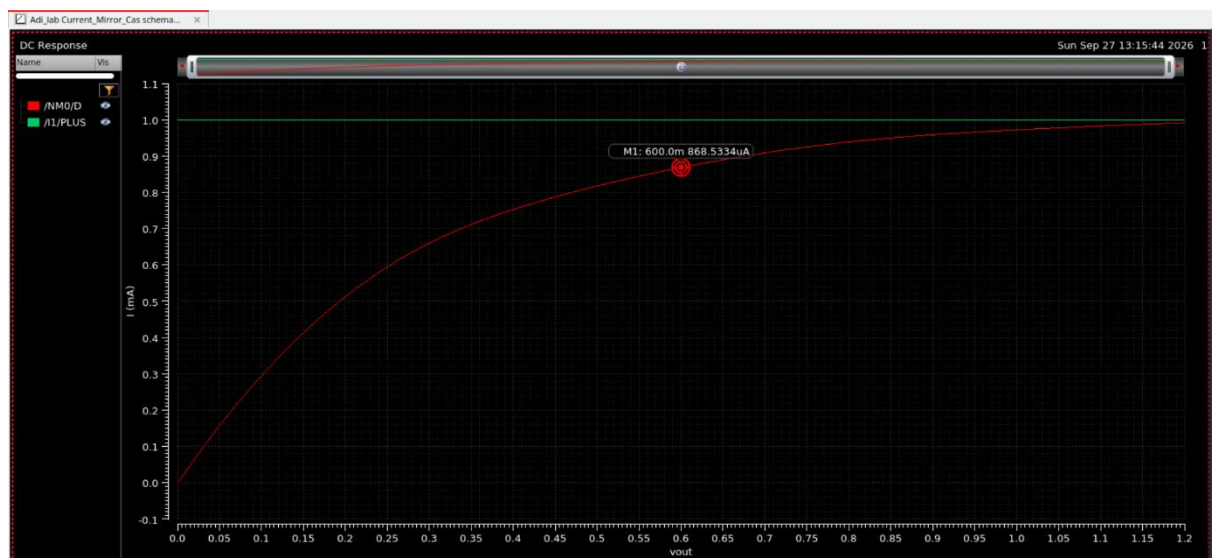

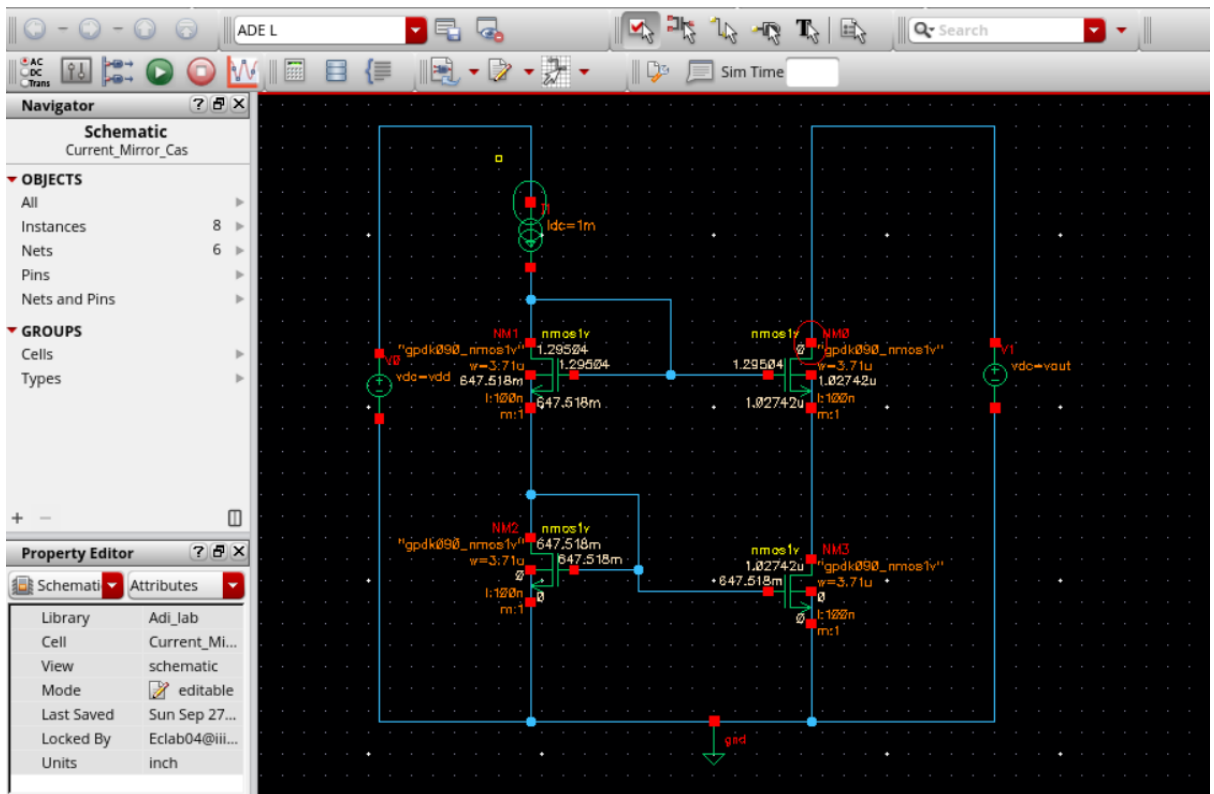

3. NMOS Characterisation result

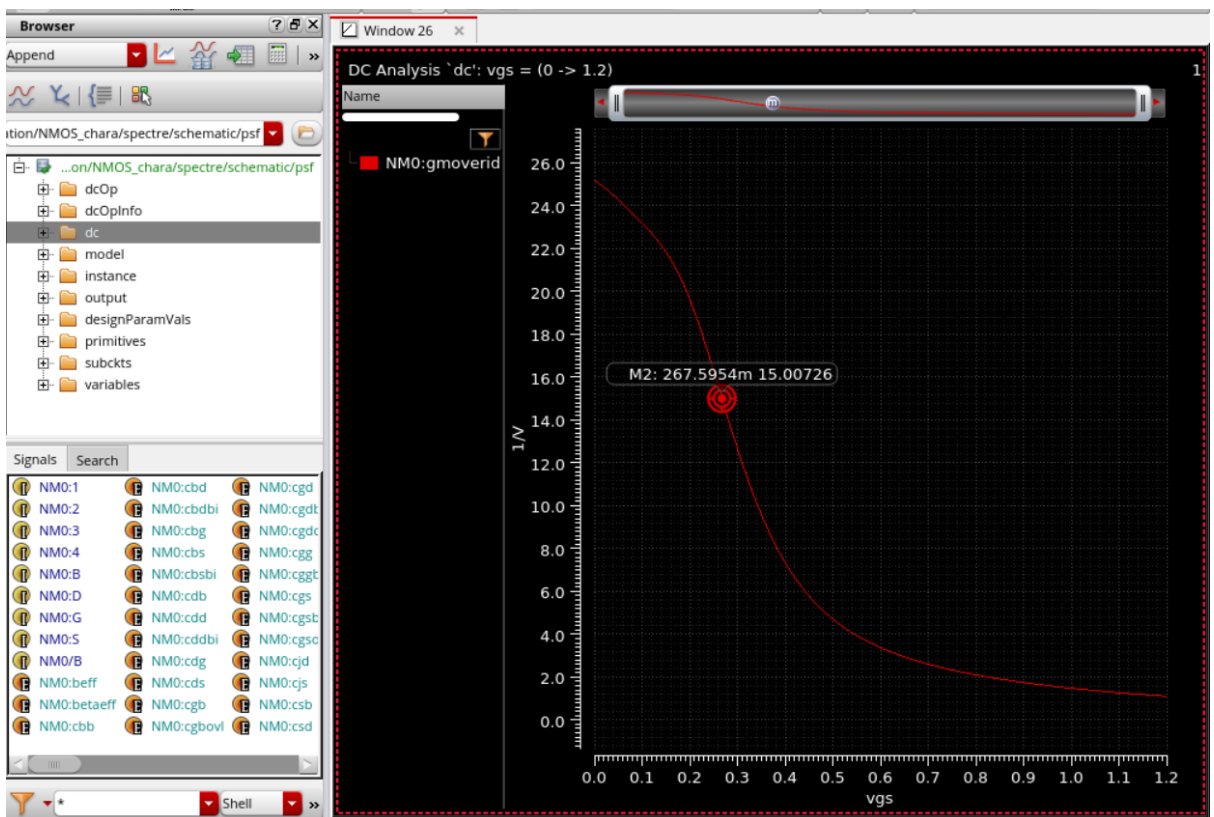

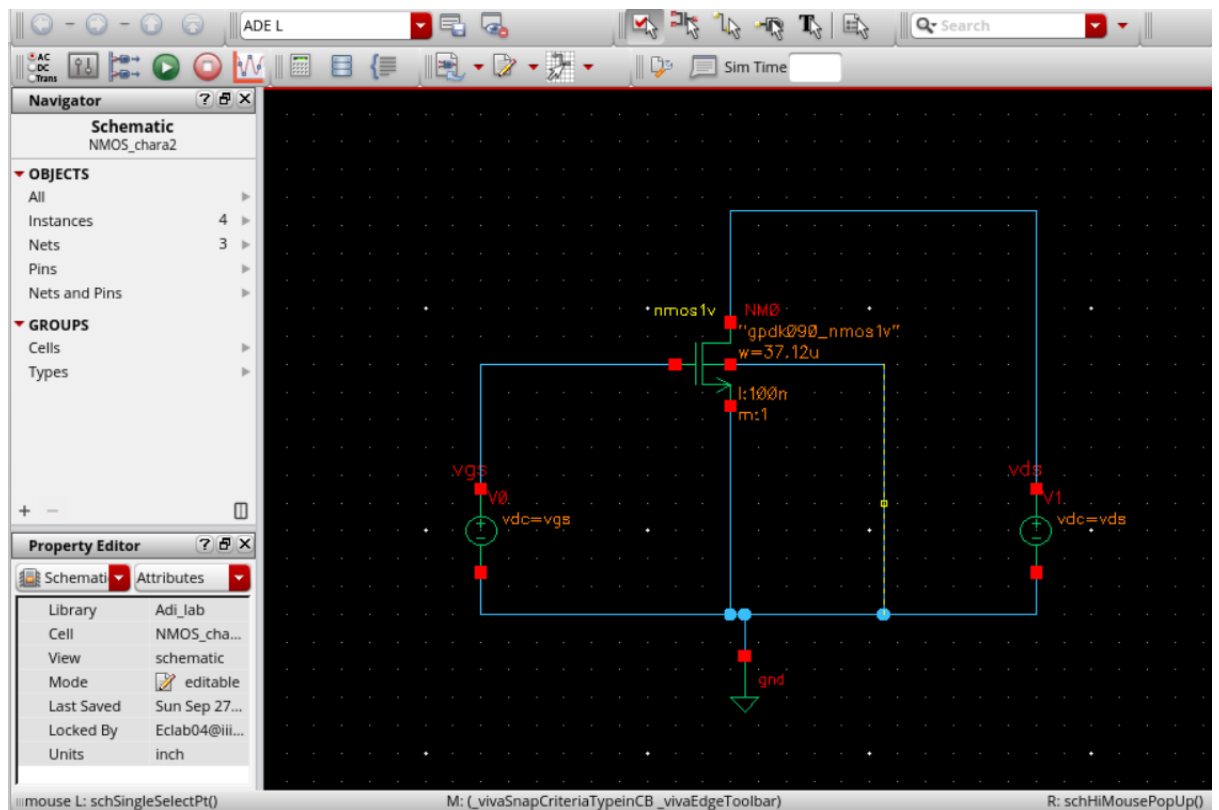

$$W = 1\mu/267.5954\text{m} = 3.71\mu$$

Fingers = 2

The advantage of Cascode current mirror over a simple current mirror is its significantly higher output resistance, which directly minimizes channel-length modulation errors and ensures a highly accurate current transfer ratio.