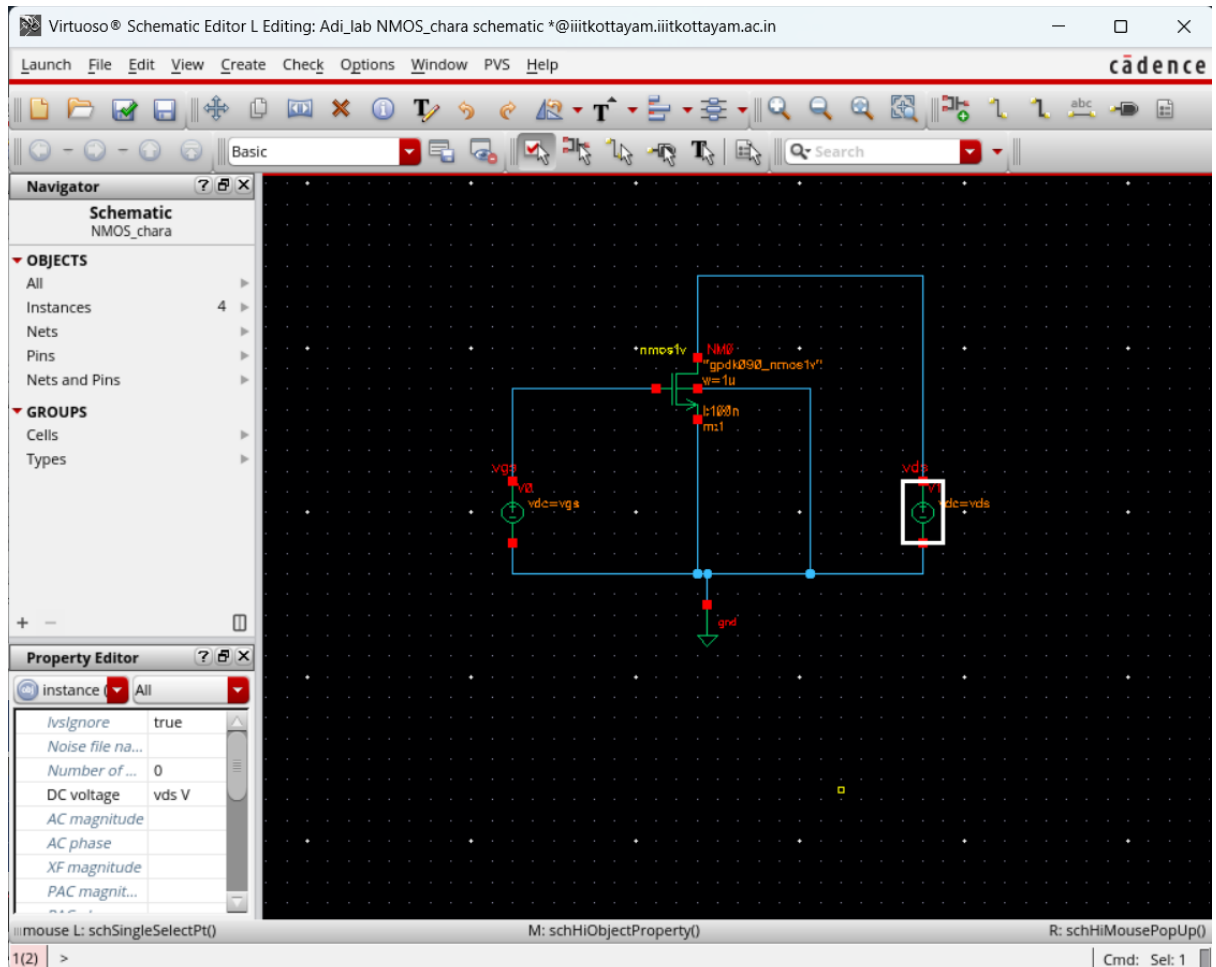


NMOS Characterization


Adithyan Anilkumar

2025BEC0014


1. Schematic




2. I_D vs V_{GS}

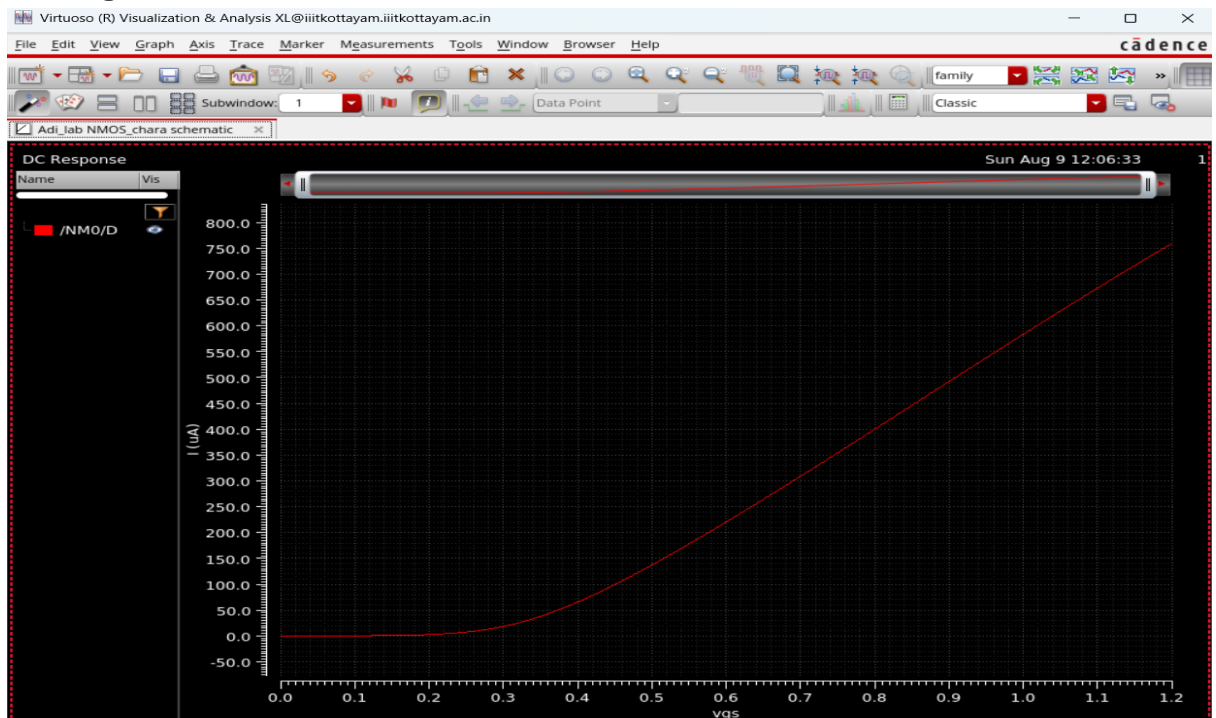

3. I vs V_{ds}

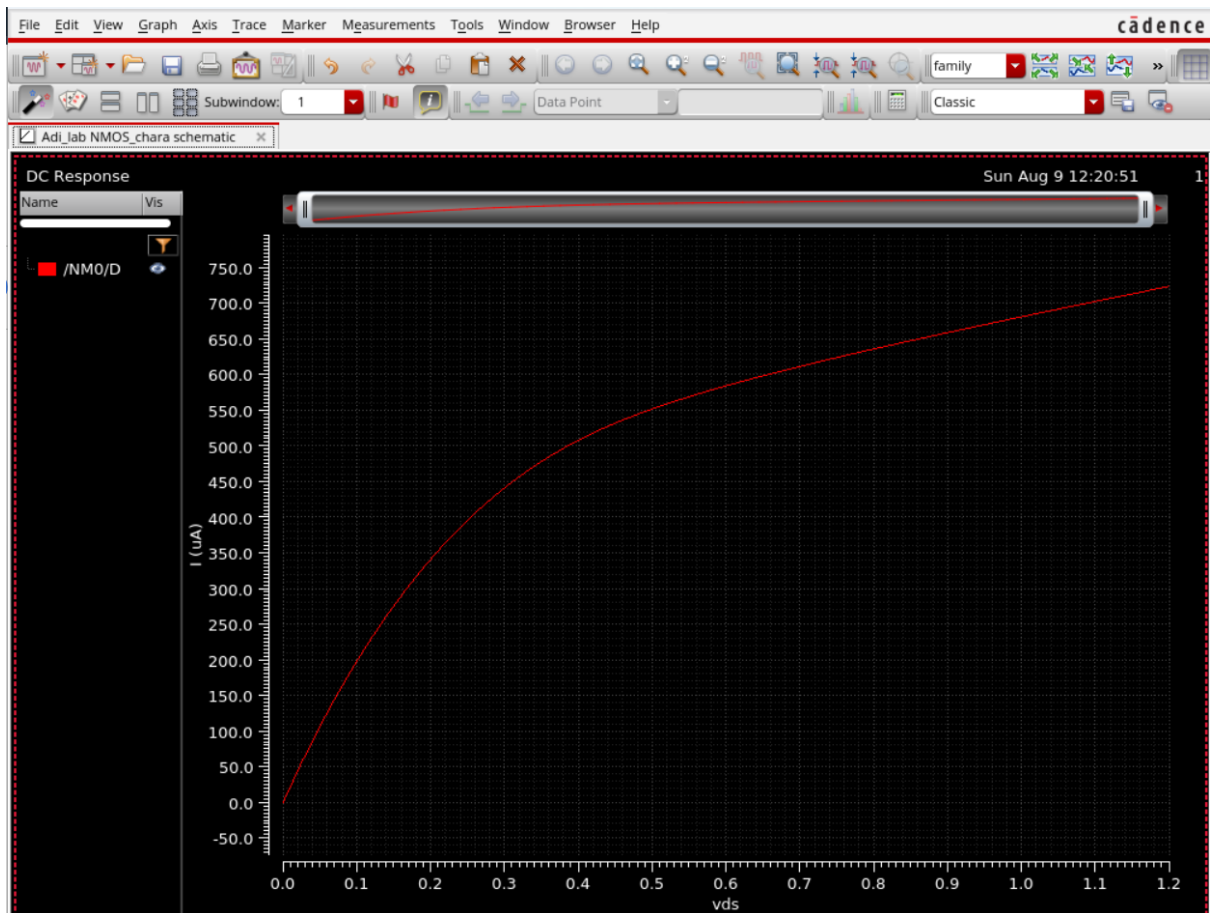

4. I vs V_{ds} Parametric

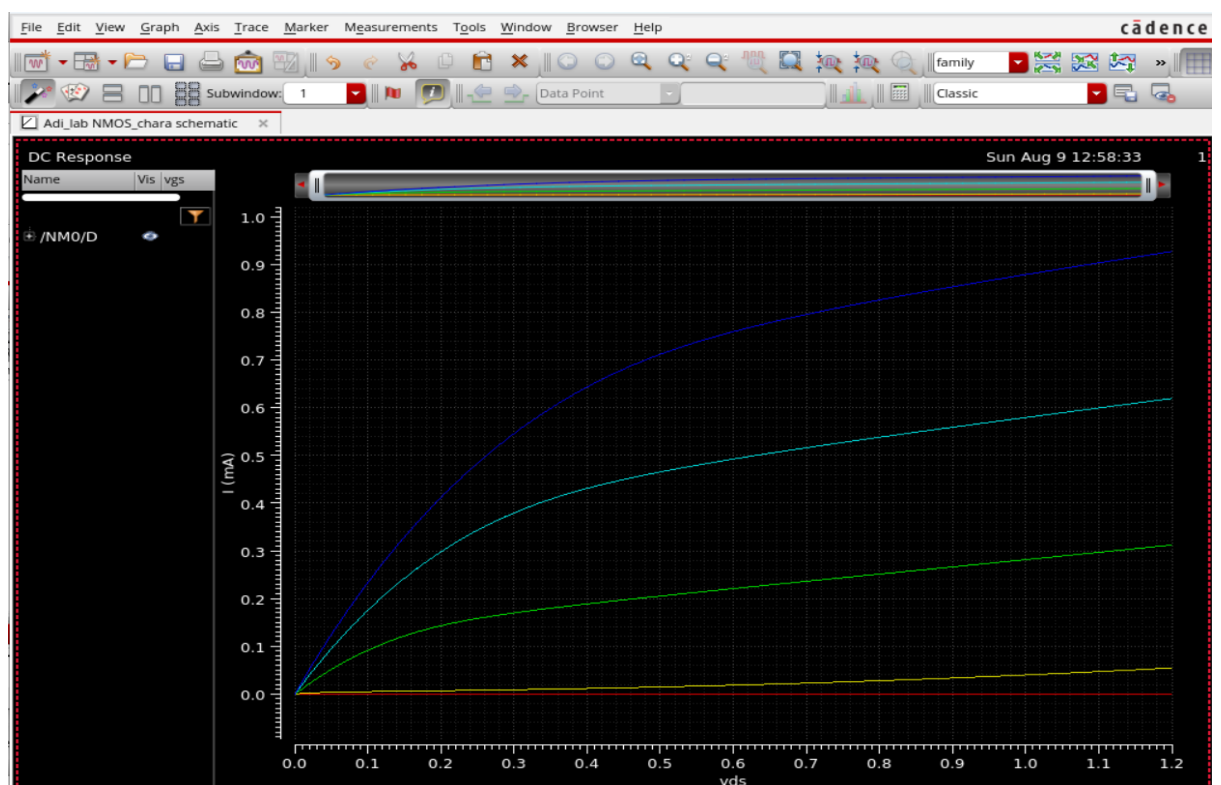

Git-Hub link

https://github.com/Adithyan-its10/AnalogElectronicsLab_2025BEC0014.git